

Enhanced PWM Circuit

Signature and Grading Sheet

Group #:_____ **Name(s):**_____.

Grading

- Section 4.1(a): VHDL code (45points):_____.
Attach code printout (with proper header and comment)
- Section 4.1(b): Block diagram (15 points):_____.
Attach diagram (can be manually drawn and photoed)
- Section 4.2(b) RT-level simulation waveform (20 points):_____.
Attach simulation waveform screen capture
- Section 4.3(e): post-synthesis simulation waveform (10 points): _____.
Attach simulation waveform screen capture
- VHDL code format and comments (10 points):_____.

Total points: _____.

Experiment

Enhanced PWM Circuit

1 Purpose

To design an enhanced PWM (Pulse Width Modulation) circuit

2 Reading


Chapter 5 of *FPGA Prototyping by VHDL Examples 2nd edition*.

3 Project specification

A PWM circuit has an output pulse whose duty cycle (i.e. the fraction of a period that is "high") is specified by a control signal. In the enhanced version, we want to control the exact time of the on and off intervals. The inputs and output of this circuit are specified as follows:

- `clk`: input clock signal. The period of `clk` is T_c .
- `d`: a 4-bit input signal. It is interpreted as an unsigned number and used to specify the "off-interval" of the pulse signal.
- `w`: a 4-bit input signal. It is interpreted as an unsigned number and used to specify the "on-interval" of the pulse signal.
- `pulse`: a 1-bit output.

 The waveform of the `pulse` signal is shown below. Note that it can be considered as a squared wave with a period of $(d+w)*T_c$ and with the $w*T_c$ portion asserted.



The design must synchronous or 50% will be deducted.

4 Design Procedures

4.1 VHDL design


The entity declaration of this design is shown below:

```
entity epwm is
  port(
    clk, reset: in std_logic;
    d, w: in std_logic_vector(3 downto 0);
    pulse: out std_logic
  );
end epwm;
```

- Derive VHDL code.
- Draw the top-level conceptual diagram (up to 10 blocks) of your code.

 4.2 Simulation

- Use the testbench (epwm_tb.vhd) to simulate your VHDL code. The testbench includes the test patterns of d=4, w=4; d=1, w=15; d=15, w=1; d=0, w=1; d=1, w=0.
- Develop a proper “layout” and “format” for the simulated waveform. To get full credits, the input and output signals should be properly arranged and represented in a proper format so that the simulation result can be easily understood (like the one below). Do a screen capture of the simulated result.



4.3 Post-synthesis ModelSim simulation

- Perform compiling (synthesis/placement and routing) and obtain the .vho file.
- Follow the format guideline to add a header to the file and verify the “structure” architecture body is generated.
- Revise the testbench to use the “structure” architecture for uut.
- Perform post-synthesis simulation
- Do a screen capture of the simulated result.
- Since the waveform is the same as the RT-level simulation, the snapshot should include the expanded **uut** on the left panel. No point will be given if the uut unit is not expanded in the snapshot.