

Thunderbird Turn Signal

Signature and Grading Sheet

Group #:_____ **Name(s):**_____.

Grading

- Section 4.1(a): FSM state diagram (15 points):_____.
Attach state diagram (can be manually drawn and then photoed)
- Section 4.1(b): ASM chart (15 points):_____.
Attach ASM chart (can be manually drawn and then photoed)
- Section 4.1(c): VHDL code (30 points):_____.
Attach code
- Section 4.2(b) RT-level simulation waveform (20 points):_____.
Attach simulation waveform screen capture.
- Section 4.3(e): post-synthesis simulation waveform (10 points): _____.
Attach simulation waveform screen capture
- VHDL code file format and comments (10 points):_____.

Total points:_____.

Experiment

Thunderbird Turn Signal

1 Purpose


To design an FSM

2 Reading


- Chapter 5 of *FPGA Prototyping by VHDL Examples*

3 Project specification

 The taillights of a 1965 Ford Thunderbird (a classic car) are shown below:



 There are three lights on each side that operate in sequence to indicate the direction of a turn. There are three flashing sequences: left turn, right turn, and hazard. The left-turn sequence is:



The right-turn sequence is similar and represents a “mirror” sequence of the left-turn pattern. In the hazard sequence, the six lights flash on and off alternatively.

A simple FSM can be constructed to control the tail light operation. The input and output are

- input:
 - clk: clock signal
 - reset: asynchronous reset signal
 - left: 1-bit left-turn signal.
 - right: 1-bit right-turn signal.
 - haz: 1-bit hazard signal.
- output
 - light: 6-bit light signal.

The system operates as follows:

- Anytime haz is asserted, the FSM enters the hazard sequence immediately. If the FSM currently in the middle of a left- or right-turn sequence, the sequence will be aborted.
- When haz is not asserted and left is asserted and, the FSM goes through the complete left-turn sequence. This means that the lights should go through a complete left-turn sequence even if left is de-asserted sometime in the middle of the sequence or if right is asserted in the middle of a sequence. However, the FSM enters the hazard sequence if haz is asserted.
- When haz is not asserted and right is asserted, the FSM goes through the complete right-turn sequence. This means that the lights should go through a complete right-turn sequence even if right is de-asserted sometime in the middle of the sequence or if left is asserted in the middle of a sequence. However, the FSM enters the hazard sequence if haz is asserted.
- We assume that left and right will never be asserted simultaneously.

The design must be synchronous, or 50% will be deducted.

4 Design Procedures

4.1 FSM

- Derive the FSM and draw the complete state diagram.
- Convert the state diagram to an ASM chart following the notations used in the lecture.
- Design the FSM in VHDL. The entity declaration of this design is


```
entity tbird_fsm is
    port(
        clk, reset: in std_logic;
        left, right, haz: in std_logic;
        light: out std_logic_vector(5 downto 0)
    );
end tbird_fsm;
```

Derive the architecture body.

4.2 Simulation

- Use the testbench (tbird_tb_2020.vhd) to simulate your VHDL code.
- Develop a proper “layout” and “format” for the simulated waveform. If needed, use multiple screen captures to make the 6-bit output patterns visible. To get full credits, the input and output signals should be properly arranged and represented in a proper format so that the simulation result can be easily understood.

(c) The expected waveform is:

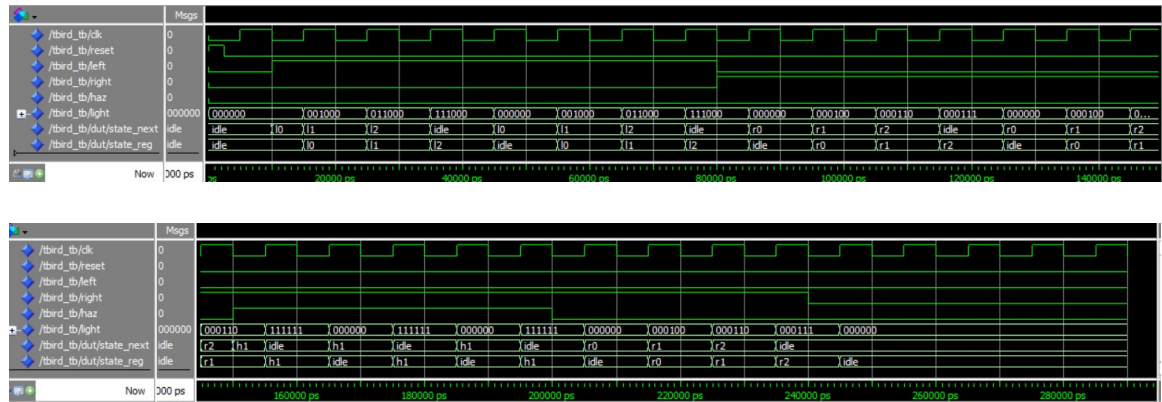

It is critical to observe the symbolic state transitions in an FSM. To include the internal state signals, expand `tbird_tb` on the left panel, select `dut` instance (i.e., `tbird_fsm` design) and drag the `state_reg` and `state_next` signals to the Wave panel. Note that your design may have different state names and even different transitions but the output should be the same.

4.3 Post-synthesis ModelSim simulation

- Perform compiling (synthesis/placement and routing) and obtain the .who file.
- Follow the format guideline to add a header to the file and verify the “structure” architecture body is generated.
- Revise the testbench to use the “structure” architecture for uut.
- Perform post-synthesis simulation. Note that the symbolic states are converted to binary representation during synthesis and thus the `state_reg` and `state_next` signals no longer exist.
- Do screen capture(s) of the simulated result.
- Since the waveform is the same as the RT-level simulation, the snapshot should include the expanded **uut** on the left panel. No point will be given if the **uut** unit is not expanded in the snapshot.